Table of Contents

CHAPTER ONE: BOOLEAN ALGEBRA AND BINARY LOGIC 1
1.1 BINARY LOGIC AND GATES 1
1.2 BOOLEAN ALGEBRA 2
1.3 Map Simplification 9
1.3.2 KMap Reduction Rules 10
1.4. Other derived gates: 16

CHAPTER TWO: Logic Gates implementation using Resistors, Diodes, and Transistors 20
2.1 Diode Logic 20
2.2 Bipolar Transistor Logic 21
2.2.1